

Physics Lab

Teacher : Ms. Farzaneh Noor Mohammadi
Student : Mr. Ramtin Kosari

Ohm's Law Analysis


October 20, 2024

Overview

Here is book of Physics Lab experiment 2, Ohm's Law overview

Experiment Info

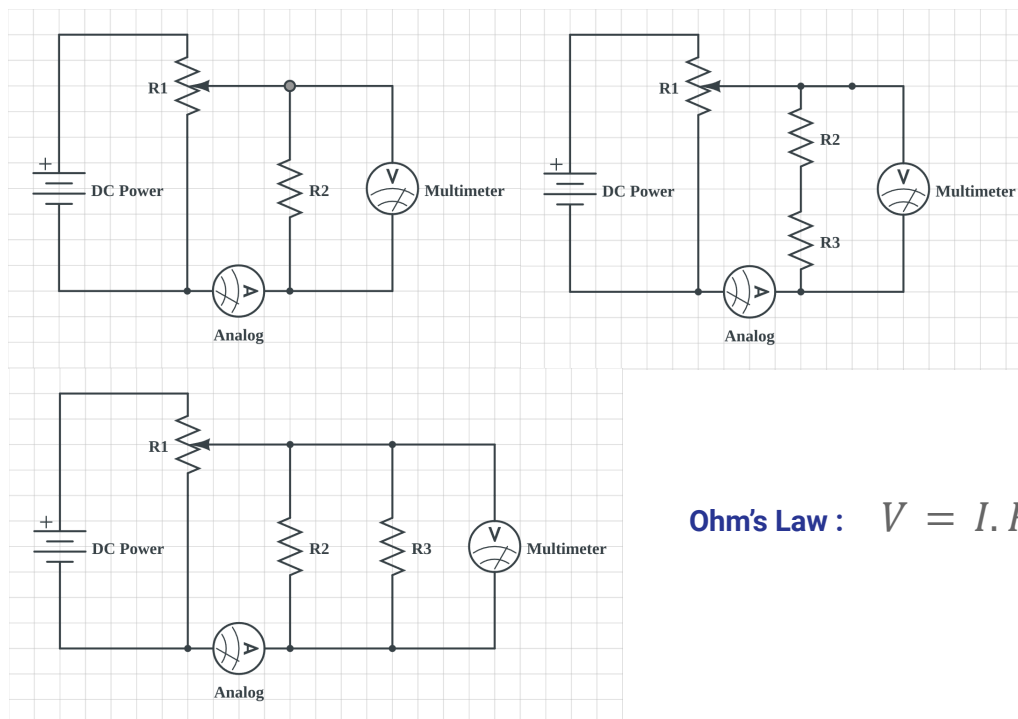- **Purpose** > Experimental Investigation of Ohm's law
- **Necessary Equipment** > Selective Resistance, DC Power, Digital Voltmeter, Analog Ammeter Wires, Rheostat




Ohm's Law : $V = I \cdot R$

Ohm's Law on Single Resistor

First we need to do this experiment on single resistor, R is a selective resistor. I conducted 2 experiments to validate Ohm's Law on a single resistor.

Steps

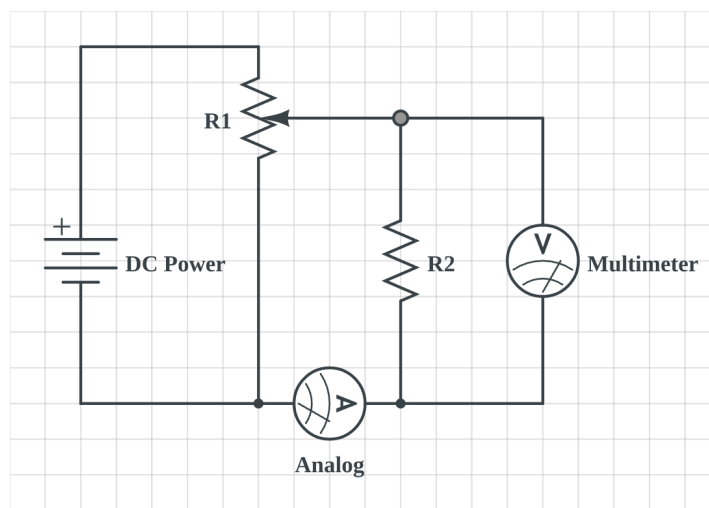1. for experiment 1, I set selective resistor on 8 so output will be $(10 - 8) * 100 = 200\Omega$ (because of using two black inputs, I used this conversion) but after connecting to multimeter I got 199.9Ω (Not $k\Omega$ because it was around 200Ω I used the first multimeter so I wrote Ω instead of $k\Omega$).
2. I set ammeter on $0.02A$ accurately.
3. Turn on DC power and enable output.
4. I set source DC power to $3.94V$ because I must configure rheostat to check $0.02A$ accurately on Ammeter.
5. Connected multimeter to R and written down its voltage, then calculated Resistor via formula and compared it to real resistor value (199.9Ω)
6. for last experiment, I only set ammeter to $0.04A$ and did the previous steps again.
7. then I changed Resistor to 9 so output will be $(10 - 9) * 100 = 100\Omega$ and multimeter showed 110.2Ω then did all the steps again.



Next pages are experiments calculations

Ohm's Law on Single Resistor - Experiments Table 1

R_{real}	V_s	I	$Ammeter_{accuracy}$	$R_{measured} = \frac{V_s}{I}$
199.9Ω	3.94V	0.02A	0.01A	197.000Ω : α
199.9Ω	7.87V	0.04A	0.01A	196.750Ω : β

Calculations of α and β :

$$\alpha : R = \frac{V_s}{I} = \frac{3.94}{0.02} = 197.000\Omega \quad \beta : R = \frac{V_s}{I} = \frac{7.87}{0.04} = 196.750\Omega$$

Ohm's Law on Single Resistor - Error Calculations

Error calculations are divided into 3 categories, absolute, relative and systematic errors and my personal task is to calculate errors of **first experiment** :

from absolute formula :

$$Absolute\ Error = |real\ value - measured\ value|$$

We get this absolute error for α :

$$\varepsilon_{abs} = |199.9\Omega - 197.0\Omega| = 2.9\Omega$$

from relative formula :

$$Relative\ Error = \frac{|real\ value - measured\ value|}{real\ value}$$

We get this absolute error for α :

$$\varepsilon_{rel} = \frac{2.9\Omega}{199.9\Omega} \approx 0.015$$

for systematic formula, We must do several mathematics operations :

1. Consider we have formula $V = I.R \Rightarrow R = \frac{V}{I}$.
2. Take the *ln* from both sides.
3. Take the **differential** from both sides.
4. Convert differentials to delta (Δ).
5. Convert every $-$ to $+$.
6. accuracy of **Analog Device** is equal to the lowest shown range on the device.
7. Error of **Analog Device** is equal to the lowest shown range on device multiplied by 0.5.

8. accuracy of **Digital Device** is equal to 10^{-x} where x is float level on the screen.
9. Error of **Digital Device** is equal to 10^{-x} where x is float level on the screen.

Now we can calculate systematic error using main formula :

$$\text{Step 1: } R = \frac{V_s}{I_{am}}$$

for R :

$$\text{Step 2: } \ln(R) = \ln(V_s) - \ln(I_{am})$$

$$\text{Step 3: } \frac{dR}{R} = \frac{dV_s}{V_s} - \frac{dI_{am}}{I_{am}}$$

$$\text{Step 4: } \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} - \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 5: } \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} + \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 6~: } \Delta V_s = 10^{-2} \quad \Delta I_{am} = 10^{-2} \times 0.5$$

$$\text{Final: } \frac{\Delta R}{R} = \frac{10^{-2}V}{3.94V} + \frac{10^{-2} \times 0.5A}{0.02A} = 0.2525$$

$$\Rightarrow \varepsilon_{sys} = 0.2525$$

Ohm's Law on Single Resistor - Experiments Table 2

R_{real}	V_s	I	$Ammeter_{accuracy}$	$R_{measured} = \frac{V_s}{I}$
110.2Ω	4.52V	0.04A	0.01A	113.000Ω : α
110.2Ω	2.10V	0.02A	0.01A	105.000Ω : β

Calculations of α and β :

$$\alpha : R = \frac{V_s}{I} = \frac{4.52}{0.04} = 113.000\Omega \quad \beta : R = \frac{V_s}{I} = \frac{2.10}{0.02} = 105.000\Omega$$

Ohm's Law on Single Resistor - Error Calculations

Error calculations are divided into 3 categories, absolute, relative and systematic errors and my personal task is to calculate errors of **first experiment** :

from absolute formula :

$$Absolute\ Error = |real\ value - measured\ value|$$

We get this absolute error for α :

$$\varepsilon_{abs} = |110.2\Omega - 113.0\Omega| = 2.8\Omega$$

from relative formula :

$$Relative\ Error = \frac{|real\ value - measured\ value|}{real\ value}$$

We get this absolute error for α :

$$\varepsilon_{rel} = \frac{2.8\Omega}{110.2\Omega} \approx 0.025$$

for systematic formula, We must do several mathematics operations :

1. Consider we have formula $V = I \cdot R \Rightarrow R = \frac{V}{I}$.
2. Take the *ln* from both sides.
3. Take the **differential** from both sides.
4. Convert differentials to delta (Δ).
5. Convert every $-$ to $+$.
6. accuracy of **Analog Device** is equal to the lowest shown range on the device.
7. Error of **Analog Device** is equal to the lowest shown range on device multiplied by 0.5.

8. accuracy of **Digital Device** is equal to 10^{-x} where x is float level on the screen.
9. Error of **Digital Device** is equal to 10^{-x} where x is float level on the screen.

Now we can calculate systematic error using main formula :

$$\text{Step 1:} \quad R = \frac{V_s}{I_{am}}$$

for R :

$$\text{Step 2:} \quad \ln(R) = \ln(V_s) - \ln(I_{am})$$

$$\text{Step 3:} \quad \frac{dR}{R} = \frac{dV_s}{V_s} - \frac{dI_{am}}{I_{am}}$$

$$\text{Step 4:} \quad \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} - \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 5:} \quad \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} + \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 6~:} \quad \Delta V_s = 10^{-2} \quad \Delta I_{am} = 10^{-2} \times 0.5$$

$$\text{Final:} \quad \frac{\Delta R}{R} = \frac{10^{-2}V}{4.52V} + \frac{10^{-2} \times 0.5A}{0.04A} = 0.1272$$


$$\Rightarrow \varepsilon_{sys} = 0.1272$$

Ohm's Law on Parallel Resistors

Now we need to do this experiment on parallel resistors, R_2 is a selective and R_3 is a box resistor. I conducted 2 experiments to validate Ohm's Law on parallel resistors.

Steps

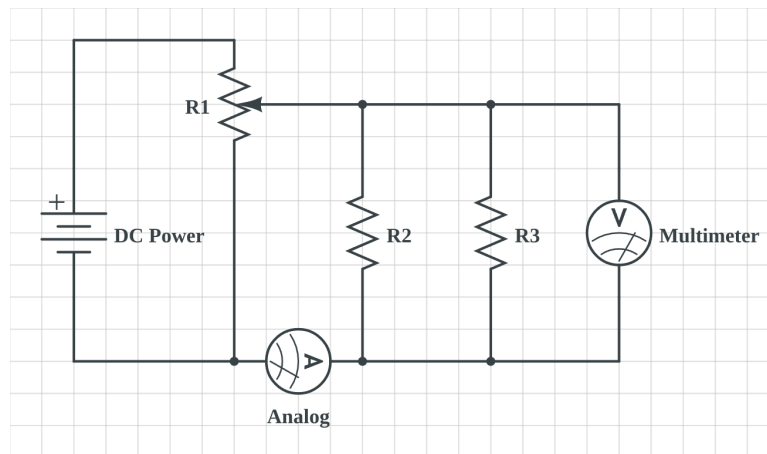1. for experiment 1, I set selective resistor on 8 so output will be $(10 - 8) * 100 = 200\Omega$ (because of using two black inputs, I used this conversion) but after connecting to multimeter I got 199.9Ω (Not $k\Omega$ because it was around 200Ω I used the first multimeter so I wrote Ω instead of $k\Omega$). also I set box resistor on 100Ω .
2. I set ammeter on $0.04A$ accurately.
3. Turn on DC power and enable output.
4. I set source DC power to $1.57V$ because I must configure rheostat to check $0.04A$ accurately on Ammeter.
5. Connected multimeter to R_3 and written down its voltage, then calculated Parallel Resistor via formula and compared it to real parallel resistor value.
6. for last experiment, I only set ammeter to $0.04A$ and did the previous steps again.



Ohm's Law on parallel Resistor - Experiments Table

R_2	R_3	$R_{real} = \frac{R_2 \times R_3}{R_2 + R_3}$	V_S	I	$Ammeter_{accuracy}$	$R_{measured} = \frac{V_S}{I}$
199.9Ω	110.2Ω	71.038Ω	1.57V	0.02A	0.01A	78.500Ω : α
199.9Ω	110.2Ω	71.038Ω	2.78V	0.04A	0.01A	69.500Ω : β

Calculations of R , α and β :

$$R_{real} = \frac{199.9 \times 110.2}{199.9 + 110.2} = 71.038\Omega$$

$$\alpha : R = \frac{V_S}{I} = \frac{1.57}{0.02} = 78.500$$

$$\beta : R = \frac{V_S}{I} = \frac{2.78}{0.04} = 69.500$$

Ohm's Law on Parallel Resistors - Error Calculations

Error calculations are divided into 3 categories, absolute, relative and systematic errors and my personal task is to calculate errors of **first experiment** :

from absolute formula :

$$Absolute\ Error = |real\ value - measured\ value|$$

We get this absolute error for α :

$$\epsilon_{abs} = |71.038\Omega - 69.500\Omega| = 1.538\Omega$$

from relative formula :

$$Relative\ Error = \frac{|real\ value - measured\ value|}{real\ value}$$

We get this absolute error for α :

$$\epsilon_{rel} = \frac{1.538\Omega}{71.038\Omega} \approx 0.022$$

for systematic formula, We must do several mathematics operations :

1. Consider we have formula $V = I.R \Rightarrow R = \frac{V}{I}$.

2. Take the \ln from both sides.
3. Take the **differential** from both sides.
4. Convert differentials to delta (Δ).
5. Convert every $-$ to $+$.
6. accuracy of **Analog Device** is equal to the lowest shown range on the device.
7. Error of **Analog Device** is equal to the lowest shown range on device multiplied by 0.5.
8. accuracy of **Digital Device** is equal to 10^{-x} where x is float level on the screen.
9. Error of **Digital Device** is equal to 10^{-x} where x is float level on the screen.

Now we can calculate systematic error using main formula :

$$\text{Step 1:} \quad R = \frac{V_s}{I_{am}}$$

for R :

$$\text{Step 2:} \quad \ln(R) = \ln(V_s) - \ln(I_{am})$$

$$\text{Step 3:} \quad \frac{dR}{R} = \frac{dV_s}{V_s} - \frac{dI_{am}}{I_{am}}$$

$$\text{Step 4:} \quad \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} - \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 5:} \quad \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} + \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 6~:} \quad \Delta V_s = 10^{-2} \quad \Delta I_{am} = 10^{-2} \times 0.5$$

$$\text{Final:} \quad \frac{\Delta R}{R} = \frac{10^{-2}V}{2.78V} + \frac{10^{-2} \times 0.5A}{0.04A} = 0.1286$$

$$\Rightarrow \varepsilon_{sys} = 0.1286$$


Ohm's Law on Series Resistors

Now we need to do this experiment on series resistors, R_2 is a selective and R_3 is a box resistor.

I conducted 2 experiments to validate Ohm's Law on parallel resistors.

Steps

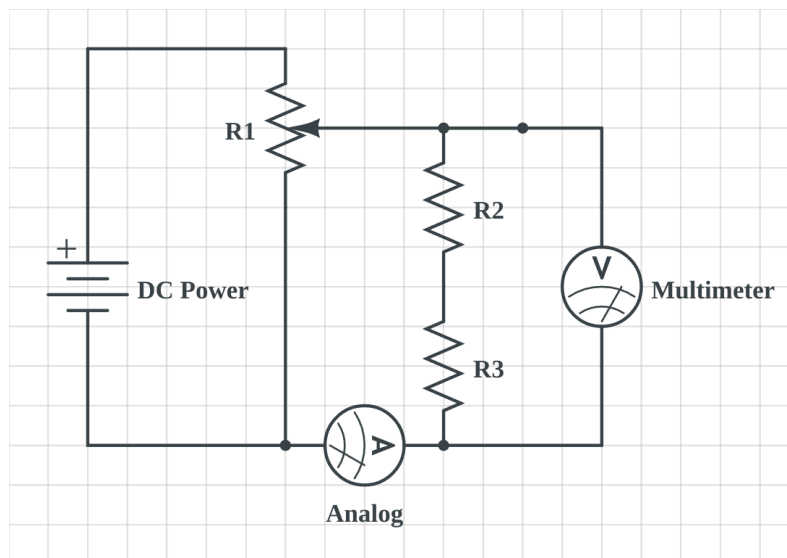1. for experiment 1, I set selective resistor on 8 so output will be $(10 - 8) * 100 = 200\Omega$ (because of using two black inputs, I used this conversion) but after connecting to multimeter I got 199.9Ω (Not $k\Omega$ because it was around 200Ω I used the first multimeter so I wrote Ω instead of $k\Omega$). also I set box resistor on 100Ω .
2. I set ammeter on $0.02A$ accurately.
3. Turn on DC power and enable output.
4. I set source DC power to $6.03V$ because I must configure rheostat to check $0.02A$ accurately on Ammeter.
5. Connected multimeter to R_3 and R_2 and wrote down its voltage, then calculated Series Resistor via formula and compared it to real parallel resistor value.
6. for last experiment, I only set ammeter to $0.04A$ and did the previous steps again.



Ohm's Law on parallel Resistor - Experiments Table

R_2	R_3	$R_{real} = R_2 + R_3$	V_s	I	$Ammeter_{accuracy}$	$R_{measured} = \frac{V_s}{I}$
199.9Ω	110.2Ω	310.100Ω	6.03V	0.02A	0.01A	301.500Ω : α
199.9Ω	110.2Ω	310.100Ω	12.24V	0.04A	0.01A	306.000Ω : β

Calculations of R , α and β :

$$R_{real} = 199.9 + 110.2 = 301.500\Omega$$

$$\alpha : R = \frac{V_s}{I} = \frac{6.03}{0.02} = 301.500\Omega \quad \beta : R = \frac{V_s}{I} = \frac{12.24}{0.04} = 306.000\Omega$$

Ohm's Law on Parallel Resistors - Error Calculations

Error calculations are divided into 3 categories, absolute, relative and systematic errors and my personal task is to calculate errors of **first experiment** :

from absolute formula :

$$Absolute\ Error = |real\ value - measured\ value|$$

We get this absolute error for α :

$$\varepsilon_{abs} = |310.100\Omega - 306.000\Omega| = 4.100\Omega$$

from relative formula :

$$Relative\ Error = \frac{|real\ value - measured\ value|}{real\ value}$$

We get this absolute error for α :

$$\varepsilon_{rel} = \frac{4.100\Omega}{310.100\Omega} \approx 0.013$$

for systematic formula, We must do several mathematics operations :

$$10. \text{ Consider we have formula } V = I \cdot R \Rightarrow R = \frac{V}{I}.$$

11. Take the \ln from both sides.

12. Take the **differential** from both sides.
13. Convert differentials to delta (Δ).
14. Convert every $-$ to $+$.
15. accuracy of **Analog Device** is equal to the lowest shown range on the device.
16. Error of **Analog Device** is equal to the lowest shown range on device multiplied by 0.5.
17. accuracy of **Digital Device** is equal to 10^{-x} where x is float level on the screen.
18. Error of **Digital Device** is equal to 10^{-x} where x is float level on the screen.

Now we can calculate systematic error using main formula :

$$\text{Step 1:} \quad R = \frac{V_s}{I_{am}}$$

for R :

$$\text{Step 2:} \quad \ln(R) = \ln(V_s) - \ln(I_{am})$$

$$\text{Step 3:} \quad \frac{dR}{R} = \frac{dV_s}{V_s} - \frac{dI_{am}}{I_{am}}$$

$$\text{Step 4:} \quad \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} - \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 5:} \quad \frac{\Delta R}{R} = \frac{\Delta V_s}{V_s} + \frac{\Delta I_{am}}{I_{am}}$$

$$\text{Step 6~:} \quad \Delta V_s = 10^{-2} \quad \Delta I_{am} = 10^{-2} \times 0.5$$

$$\text{Final:} \quad \frac{\Delta R}{R} = \frac{10^{-2}V}{12.24V} + \frac{10^{-2} \times 0.5A}{0.04A} = 0.1258$$

$$\Rightarrow \varepsilon_{sys} = 0.1258$$

Result

1. We proved Ohm's Law for single, parallel and series resistors.

